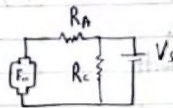


transformer 11 grade


DC Machine [Generator - Motor]

* DC machine
 I not exist
 R not exist
 E not exist
 S not exist
 $P = I \times V$



DC Generator

* Generator (mech → electrical)

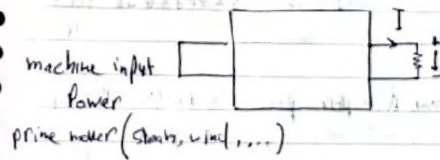

$$P_{out} = V \times I$$

$$R = \frac{V}{I}$$


التيار
 $N \cdot I$

$$P_{in} = I \times W = \text{watt}, \quad n, \text{rpm revolution/second}$$

$$1 \text{ rpm} = \frac{2\pi}{60}, \quad n \text{ rpm} = \frac{n \cdot 2\pi}{60}$$

Generator Action



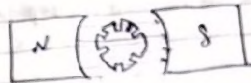



[P]: number of Poles [even]

[C]: number of coils



[N_c]: number of turn per coil

[Z]: number of conductors $Z = (C)(N)$

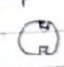[Single Layer Machine]: number of coils equal to half number of slots
coil per 2 slots 

[Double layer machine]: number of coils equal to number of slots 

Winding

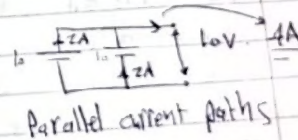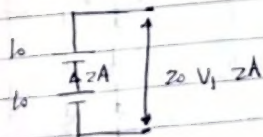

Parallel current paths

Armature Winding of DC-Machine

Lap winding $q = mP$ q : number of paths
 P : number of poles
 m : $m=1$ simplex, $m=2$ duplex, $m=3$ triplex

Wave Winding $q = 2m$


Ex: a DC machine have 24 slot, its a Single Layer, Simplex Lap Winding and it has 2 poles

Single Layer $\Rightarrow 12$ coil

simplex $m=1$

Lap winding $a = mp = (1)(2) = 2$ paths

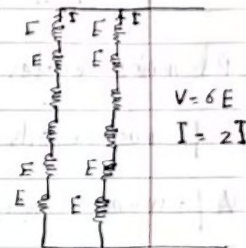Since we have 2 paths $12/2 = 6$ coil/path




[b] if number of poles = 4, Since Lap winding, slot 24, single layer, simplex

- 12 coil

- $m=1$

- Lap $a = mp = (1)(4) = 4$ Paths

$12/4 = 3$ coil / Path

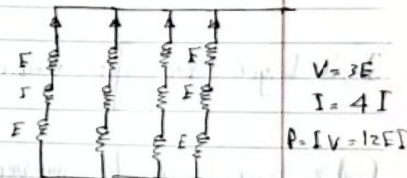

if $R_{coil} = 1 \Omega$, $R_{path} = R_{coil} + R_{coil} + R_{coil} = 3 \Omega$

$$\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3} + \frac{1}{3} = \frac{4}{3}$$

$$R_{eq} = \frac{3}{4} \Omega$$


[c] if Single Layer Simplex Wave Winding, with 24 slot, 4 pole

Single $\Rightarrow 12$ coil

Simplex $m=1$

wave $a = 1 = 24/12 = 2$ Paths

$12/2 = 6$ coil / Path

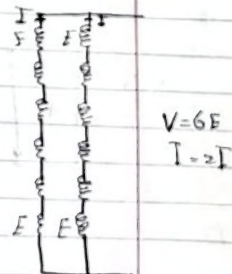


$$R_{eq} = \frac{R_{path}}{n \text{ path}}$$

Armature Resistance :

$$R_{coil} = N_c R_{turn}$$

$R_{conductor}$

$$[R_{turn} = 2 R_{conductor}]$$

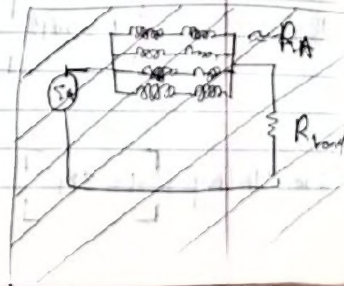

iV at, 10
 ov bl, 5
 ad al, 1

10 10
 al al


zero and
 $\neq 0$

$\Gamma_{01} [\Gamma_{02}] \Delta z \Gamma_0 \Delta z$

ov al
 ov bl
 nd al


Ex: number of coil = 48, $P = 4$ poles, Lab winding each coil has 10 turns each turn has a Resistance value with 0.01Ω , simplex

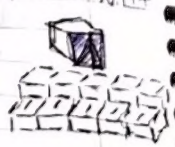- 48 coil - 10 turns/coil - $R_{turn} = 0.01 \Omega$
 - 4 poles
 - Lab $\rightarrow a = mP = (1) (4) = 4$ Poles
 - simplex $\rightarrow m = 1$
 $R_{coil} = 10 \times 0.01 = [0.1 \Omega]$, $R_{path} = 12 \times 0.1 = [1.2 \Omega]$



$48 / 4 = 12 \text{ coil/path}$

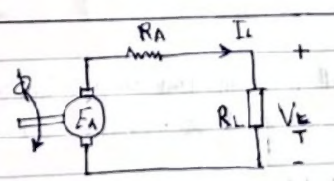$1 / R_{eq} = \frac{1}{1.2} + \frac{1}{1.2} + \frac{1}{1.2} + \frac{1}{1.2} = \frac{4}{1.2}$, $\left[\frac{R_{eq} = 1.2}{A_{eq} = 4} \right] = \frac{R_{path}}{No path}$



$\phi_{flux} = Wb \text{ or } V/s$

W : Speed (rad/s), it need to be in rpm
 $n \text{ rpm} = \left[\frac{n 2\pi}{60} \right] \text{ (rad/s)}$

$E = K \phi W$

K : mechanical constant

$\left[K = \frac{ZP}{2\pi a} \right]$, $Z = ZCN$, $P = no. of poles$

E : induced voltage

$V_T = E_A - I_A R_A$

* التيار منفرقا من E_A على V_T \rightarrow E_A منفرقا عن طرفين ϕ او ϕ او ϕ

V_T : Terminal voltage

Voltage Regulation, DC-generator

$V_R = \frac{E_A - V_T}{V_T} \times 100\%$

Example: DC generator has 80 coils each coil with 4 turns
 Simplex Lap winding, $P = 4$ poles, if armature Resistance $R_A = 0.5 \Omega$
 Determine the following if the $\phi = 0.04 \text{ Wb}$

1- No Load Voltage if the generator Prime mover = 1000 rpm

2- Determine the Speed required the generator supplied at load of 4KW, $V_T = 500 \text{ V}$

- 80 coils - 4 turn/coil - 4 poles
- Simplex $m = 1$
- Lap $a = mp = (1)(4) = 4 \text{ paths}$
- $R_A = 0.5 \Omega$
- $\phi = 0.04 \text{ Wb}$
- $Z = (4)(80)(90) = 720$



[a] - at no load $I_A = 0$ close to being zero so small to point that we can ignore it

$$V_T = E_A - I_A R_A$$

$$\phi = 0.04 \text{ Wb}$$

$$V_T = E_A = K \phi W, \quad K = \frac{ZP}{2\pi a} = \frac{(720)(4)}{2\pi(4)} = 114.591559$$

$$W = \left(\frac{1000}{60} \right) \frac{2\pi}{60} = 104.7197551 \text{ rad/s}$$

$$V_T = E_A = (0.04)(114.591559)(104.7197551) \approx 480 \text{ V}$$

$$[b] \quad V_T = E_A - I_A R_A$$

$$P_{\text{load}} = V_T I_A \quad I_A = \frac{4000}{500} = 8 \text{ A}$$

$$E_A = K \phi W$$

$$E_A = V_T + I_A R_A = 500 + (8)(0.5)$$

$$E_A = 504 \text{ V}$$

$$W = \frac{E_A}{K \phi} = \frac{504}{(0.04)(114.591559)}$$

$$W = \text{ans} \times \frac{60}{2\pi} = 1050 \text{ rpm}$$

Example: DC-generator, 4 poles, ~~100 A~~, $\phi = 0.02 \text{ Wb}$
 10 turn per coil, 120 slots, Single layer, $R_{turn} = 0.01 \Omega$, Simplex

- 1 - Determine Armature Resistance
- 2 - number of coils 4 - coil/paths
- 3 - number of paths

2 - Determine the induced voltage if the generator speed = 1200 rpm

3 - Determine the terminal voltage of the generator loaded by $R = 10 \Omega$

4 - Determine the Speed required for the generator to supply a load of 20 KW and $V_T = 500 \text{ V}$

5 - if the flux Induced by 50% determine the speed required for the generator to develop $E_A = 515 \text{ V}$

1. $R_{turn} = 0.01 \Omega$

$R_{coil} = (0.01) \times 10 = 0.1 \Omega$

$R_{path} = (0.1) \times 15 = 1.5 \Omega$

$R_A = \frac{1.5}{4} = 0.375 \Omega$

$R_A = 0.375 \Omega$

$R_{eq} = \frac{1.5}{4}$

10 turn per coil

$\frac{60}{4} = 15 \text{ coil/paths}$

2. $V_T = E - I_A R_A$, $E = K \phi \omega$

$E = \frac{PZ}{2\pi a} \phi \frac{1200}{60} \frac{2\pi}{60} = \frac{(4)(2 \times 10 \times 60)}{2\pi(4)} \times (0.02) \times \frac{1200 \times 2\pi}{60}$


$E = 480 \text{ V}$

$\phi = \frac{1}{2} \omega \cdot \frac{1}{\omega} \cdot \frac{1}{\omega} \cdot \frac{1}{\omega}$
 $\omega = 2\pi \cdot f$
 $\phi = \frac{1}{2} \cdot 2\pi \cdot f \cdot \frac{1}{\omega} \cdot \frac{1}{\omega} \cdot \frac{1}{\omega}$
 $\phi = \frac{1}{2} \cdot 2\pi \cdot f \cdot \frac{1}{\omega^3}$
 $\phi = \frac{1}{\omega^2}$

Zero speed
→ 0

→ 1 [200] 11 11 11

DC-Generator [generate electricity]

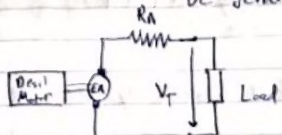

mechanical power \rightarrow P_{out} (electrical)
 $(T_{applied} \cdot \omega)$ \rightarrow Friction loss \rightarrow electrical loss \rightarrow P_{out}
 $[I_A^2 R_A]$
 $P_{out} = P_{developed} = T_{induced} \cdot \omega$
 $P_{in} = P_{loss} + P_{out}$
 $E_A \cdot I_A = P_{out loss} + P_{out electric}$

$T_{applied} = T_{input}$ $\omega \cdot T_{input} = P_{input}$ $T_{input} = \frac{P_{input}}{\omega}$ $T_{induced} = \frac{E_A \cdot I_A}{\omega}$ $T_{induced} = \frac{K \phi \omega \cdot I_A}{\omega}$	in generation $T_{app} \rightarrow T_{ind}$ $P_{app} \rightarrow P_{ind}$ $P_{in} \rightarrow P_{out}$ $P_{developed} = T_{induced} \cdot \omega$ $P_{input} = P_{loss} + P_{output}$	$T_{induced} = T_{ind}$ $\omega \cdot T_{output} = P_{output}$ $T_{induced} = \frac{P_{output}}{\omega}$ $T_{induced} = \frac{V_T \cdot I_A}{\omega}$
---	--	--

$T_{induced} = K \phi I_A$
 $\omega \cdot T_{imp} = P_{loss} + P_{output}$
 $T_{input} = \frac{P_{loss} + P_{output}}{\omega}$
 $T_{input} = \frac{P_{loss} + P_{output}}{\omega} + T_{induced}$

Δ سرعة اللف W من الدورات [rev/min] [rad/s]

Example: A DC-generator with wave simplex Lap winding with 4 poles.
 $R_A = 0.25 \Omega$ number of coils = 80 $Z = 640$ conductor

- 1- Determine Induced voltage E_A if the generator loaded by 3KW 150V
- 2- Determine the Speed required for the generator to supply load in case (1) if the flux is 0.02 Wb
- 3- Determine Induced torque for case 1 and 2

4- Determine (T_{app}) if the friction losses amounts to 100W

5- if the induced voltage $E = 160V$ and $R_A = 5\Omega$ determine T_{ind}

① $P = 4$ poles $Z = 640$ conductor

Simplex $m=1$ $N = 640 / (2)(80) = 4$ turns/coil

Lap $a = mP = (1)(4) = 4$ paths

80 coil

$\frac{80}{4} = 20$ coil/path

$$\text{① } E_A = K \phi W \quad P_{out} = I_A V_T \quad I_A = \frac{3000}{150} = 20 A$$

$$V_T = E_A - I_A R_A \quad E_A = 150 + (20)(0.25) = 155 V$$

$$\text{② } W = \frac{E}{\phi K} = \frac{155}{(0.02) \left(\frac{640 \times 4}{2\pi(4)} \right)} = \frac{60}{2\pi} = 726.5625 \text{ rev per minute}$$

$$\text{③ } T_{ind} = \frac{P_{mech}}{W} = \frac{E \cdot I_A}{W} = \frac{155 \times 20}{726.5625 \times \frac{2\pi}{60}} = 40.74 \text{ N.m}$$

$$\text{OR } T_{ind} = K \phi I_A = 40.74 \text{ N.m}$$

$$\text{④ } T_{app} = T_{ind} + \frac{P_{friction}}{W} = 40.74 + \frac{100}{726.5625 \times \frac{2\pi}{60}} = 42.054 \text{ N.m}$$

ax, 10
bl, 5
al, 1

$$E_A = V_t + V_{\text{ind}} = I_A R_L + I_A R_A = I_A (R_L + R_A)$$

$$I_A = \frac{E_A}{R_L + R_A} = \frac{160}{5 + 0.25} = 30.4 \text{ A}$$

$$T_{\text{ind}} = \frac{P_{\text{me}}}{\omega} = \frac{E_A I_A}{\omega} = K \phi \omega I_A = K \phi I_A = (0.02) (30.4) \left(\frac{60}{2\pi} \right)$$

$$T_{\text{ind}} = 62.08 \text{ N.m}$$

$$T_1 = K \phi I_{A1}$$

$$T_2 = K \phi I_{A2}$$

$$\frac{20}{30.4} = \frac{40.74}{T_2}$$

$$T_2 = 61.9$$

DC-Generator with field circuit


N.118

Permanent Magnet

electro Magnet

* Flux (ϕ) not controlled
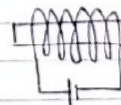
$$\phi = \frac{\text{MMF}}{R} = \frac{NI}{R}$$



field circuit: where the flux produced in DC-Generator
Armature circuit: where it deliver the current to the load

$$\phi \rightarrow I_f, [I_f \uparrow \Rightarrow \phi \uparrow, I_f \downarrow \Rightarrow \phi \downarrow]$$